 




University of Jordan  
Faculty of Engineering and Technology  
Department of Computer Engineering  
Digital Logic Laboratory 0907234


## Labsheet6: Arithmetic Circuits Simulation



Name:

Student ID:

Section:

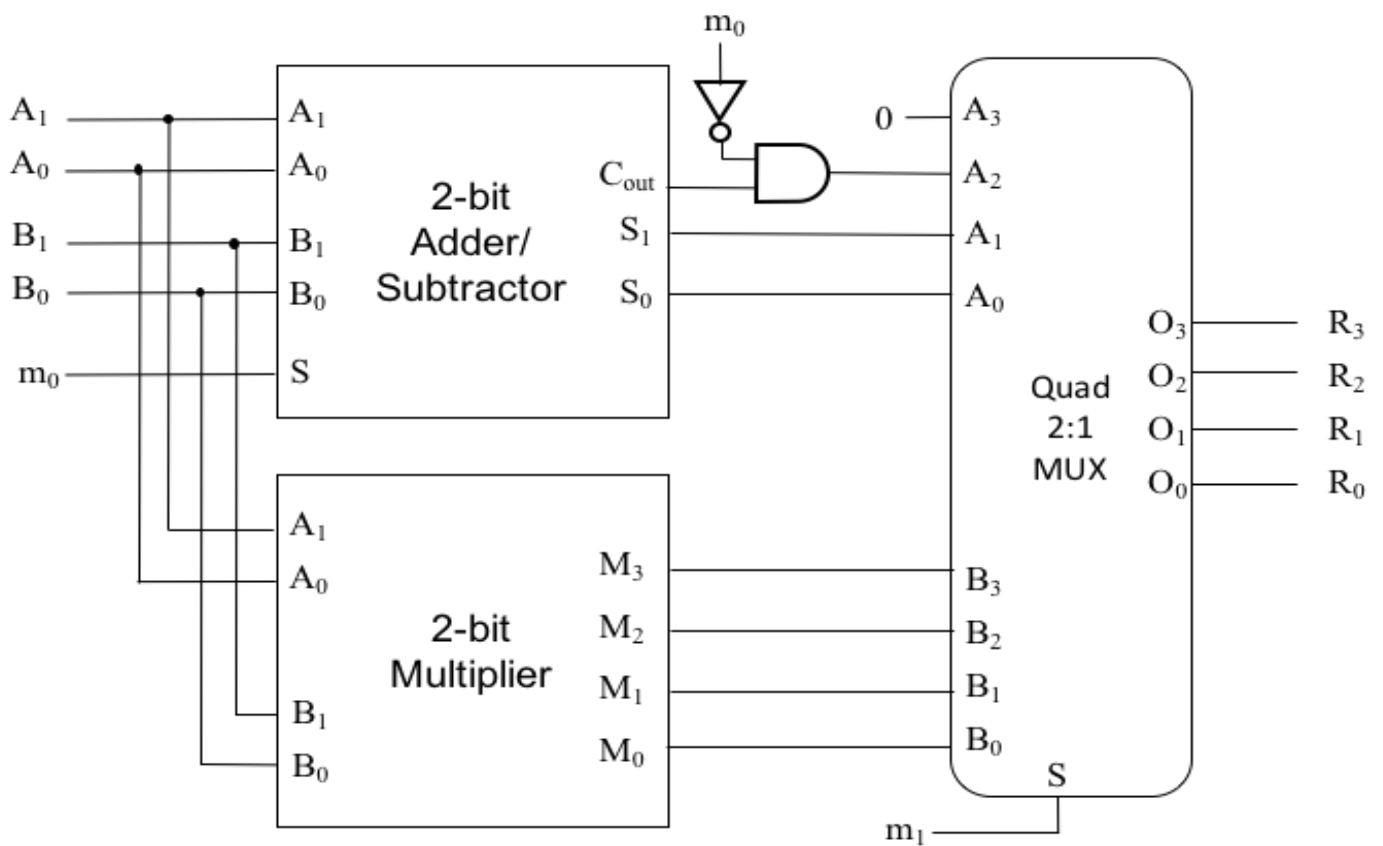

**Figure1.** 2-bit ALU Circuit

$m_1$	$m_0$	Arithmetic Operation
0	0	Addition (+)
0	1	Subtraction (-)
1	x	Multiplication (*)

**Figure2.** ALU Operations


In this experiment, our goal is to design a simple 2-bit ALU combinational circuit that perform the following unsigned operations: addition, subtraction and multiplication. As shown by Figure 1, the ALU circuit has two 2-bit unsigned input numbers A { $A_1A_0$ } and B { $B_1B_0$ } and a 4-bit unsigned output number R { $R_3R_2R_1R_0$ }. The ALU circuit also has 2-bit control signal  $m_1m_0$  that are used to choose the ALU operation (see Figure 2).

The experiment is divided into four parts. First, you will implement the quad 2-to-1 multiplexer. Second, you will implement a 2-bit ripple-carry adder/subtractor. Third, you will implement a 2-bit multiplier. Finally, you will combine all the aforementioned modules to implement the ALU circuit.

## Part1: Quad 2-to-1 Multiplexer

- a) Write the Boolean equation of the output of the 2-to-1 Multiplexer:


OUT=

 

- b) Inside `Mux2to1.v` file, write a behavioral Verilog code to implement the 2-to-1 multiplexer module. This module has 3 inputs (I0, I1 and S) and one output (OUT).
- c) Using four instances of 2-to-1 multiplexer, design a circuit of a quad 2-to-1 multiplexer.
- d) Inside `QuadMux2to1.v` file, write a structural Verilog code to implement the quad 2-to-1 multiplexer module based on your design in part c. This module has nine inputs (A3, A2, A1, A0, B3, B2, B1, B0 and S) and four outputs (O3, O2, O1 and O0).

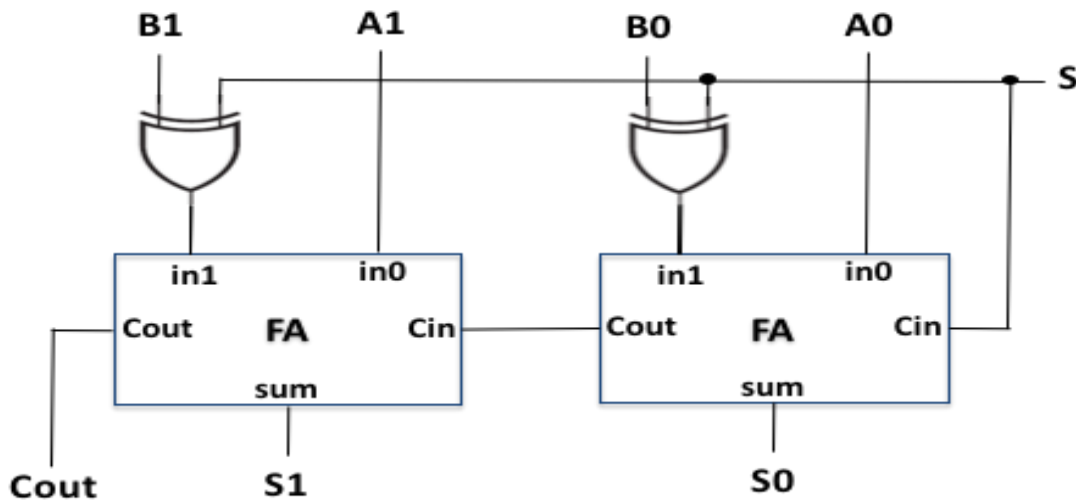
## Part2:The 2-bit Adder/Subtractor

An adder/subtractor circuit can be built using two cascaded full adders (see the figure below).



- a) Write the Boolean equations of the outputs of the full adder (FA) circuit:


sum=  
Cout=

 

- b) Inside **FA.v** file, write a behavioral Verilog code to implement the full adder module. This module has 3 inputs (in0, in1 and Cin) and 2 outputs (sum and Cout).
- c) Inside **TwoBitAdderSubtractor.v** file, write a structural Verilog code to implement the 2-bit adder/subtractor module shown by the above figure. This module has five inputs (A0,A1,B0, B1,and S) and three outputs (S0, S1 and Cout).
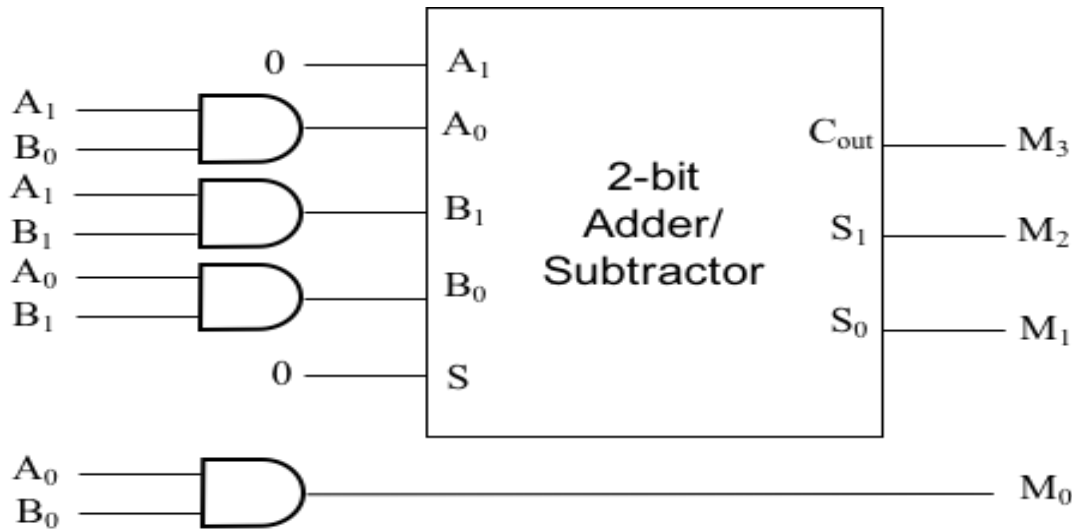
### Part3: The 2-bit Multiplier.

A 2-bit multiplication circuit can be built using four instances of AND gates and one instance of the 2-bit adder/subtractor circuit we implemented in Part1.



- a) Inside **TwoBitMultiplier.v** file, write a structural Verilog code to implement the 2-bit multiplier module shown by the above figure. This module has four inputs (A0, A1, B0, and B1) and four outputs (M0, M1, M2 and M3).

### Part4:ALU circuit design.

- a) Inside **ALU.v** file, write a structural Verilog code to implement the full ALU circuit module. For convenience, we will use **four 7-segment displays** to show the values of the operand A, operand B, the operation, and the result. Inside **segdriver2.v** and **segdriver4.v** files, we already have written the two 7-segment driver modules that you need.

The ALU circuit has the following inputs and outputs:

- 6-inputs (A0, A1, B0, B1, m0, m1)
- 28-Outputs:
  - ❖ The outputs 'a0, b0, c0, d0, e0, f0, g0', which will be connected to the 7-segment display of operand A {A<sub>1</sub>A<sub>0</sub>}.
  - ❖ The outputs 'a1, b1, c1, d1, e1, f1, g1', which will be connected to the 7-segment display of operand B {B<sub>1</sub>B<sub>0</sub>}.
  - ❖ The outputs 'a2, b2, c2, d2, e2, f2, g2', which will be connected to the operation selection lines {m<sub>1</sub>m<sub>0</sub>}.

- ❖ The outputs 'a3, b3, c3, d3, e3, f3, g3', which will be connected to the 7-segment display of the result {R<sub>3</sub>R<sub>2</sub>R<sub>1</sub>R<sub>0</sub>}

b) Make the pins assignment for the ALU circuit's inputs and outputs, as follows:

<b>Hex (0): Operand A</b>		
a0	oHEX0_D[0]	PIN_AE8
b0	oHEX0_D[1]	PIN_AF9
c0	oHEX0_D[2]	PIN_AH9
d0	oHEX0_D[3]	PIN_AD10
e0	oHEX0_D[4]	PIN_AF10
f0	oHEX0_D[5]	PIN_AD11
g0	oHEX0_D[6]	PIN_AD12
<b>Hex (1): Operand B</b>		
a1	oHEX1_D[0]	PIN_AG13
b1	oHEX1_D[1]	PIN_AE16
c1	oHEX1_D[2]	PIN_AF16
d1	oHEX1_D[3]	PIN_AG16
e1	oHEX1_D[4]	PIN_AE17
f1	oHEX1_D[5]	PIN_AF17
g1	oHEX1_D[6]	PIN_AD17
<b>Hex (2): Operation</b>		
a2	oHEX2_D[0]	PIN_AE7
b2	oHEX2_D[1]	PIN_AF7
c2	oHEX2_D[2]	PIN_AH5
d2	oHEX2_D[3]	PIN_AG4
e2	oHEX2_D[4]	PIN_AB18
f2	oHEX2_D[5]	PIN_AB19
g2	oHEX2_D[6]	PIN_AE19
<b>Hex (3): Result</b>		
a3	oHEX3_D[0]	PIN_P6
b3	oHEX3_D[1]	PIN_P4
c3	oHEX3_D[2]	PIN_N10
d3	oHEX3_D[3]	PIN_N7
e3	oHEX3_D[4]	PIN_M8
f3	oHEX3_D[5]	PIN_M7
g3	oHEX3_D[6]	PIN_M6
<b>Input Switches</b>		
A0	iSW[1]	PIN_AB26
A1	iSW[2]	PIN_AB25
B0	iSW[3]	PIN_AC27
B1	iSW[4]	PIN_AC26
m0	iSW[5]	PIN_AC24
m1	iSW[6]	PIN_AC23

c) Download your Verilog program on FPGA and test your code.